


## Design a Common Source Amplifier to achieve the following specs

Spec.	
DC Gain	0 dB
BW	≥ 30 GHz
Power Consumption	≤ 1.7 mW
Cap Load	70 fF

$$\begin{split} P_{cons} &= V_{DD} \ I_D \leq 1.7 \ mW \to I_D \leq 1.4 \ mA \\ GBW &= \frac{g_m}{2\pi C_{out}} \geq 1*30 \ GHz \to g_m \geq 13.2 \ mS \\ g_m &= 21 \ mS \to \frac{g_m}{I_D} = 15 \\ A_v &= g_m R_{out} = 1 \to R_{out} = 50 \ \Omega \to R_D = 55 \ \Omega \\ R_{out} &= \frac{R_D. \ r_o}{R_D + r_o} = 50 \to r_o \geq 550 \ \Omega \to \frac{g_m}{g_{ds}} \geq 11.55 \\ V_{DS} &= V_{out} = V_{DD} - I_D * R_D = 1.2 - 1.4 m * 55 = 1.123 \ V \\ V_{SB} &= 0 \end{split}$$

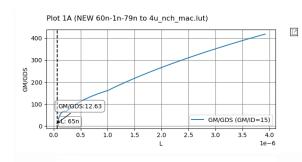


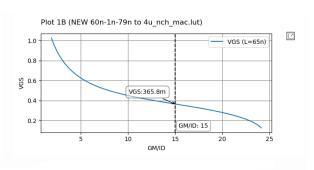

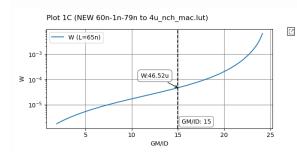

## Simulations

## DC Operating Points

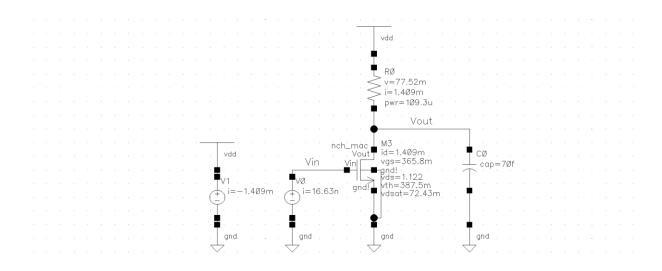

## AC Analysis

