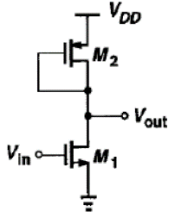


Design a single ended amplifier shown in the fig to achieve the following specs

Spec.		
DC Gain	6 dB	
BW	≥ 10 GHz	
Power Consumption	≤ 1.5 mW	
Cap Load	50 fF	

$$P_{\text{cons}} = V_{DD} I_D \leq 1.5 \text{ mW} \rightarrow I_D \leq 1.25 \text{ mA}$$

$$GBW = \frac{g_{m1}}{2\pi C_{\text{out}}} \geq 2 * 10 \text{ GHz} \rightarrow g_{m1} \geq 6.28 \text{ mS}$$





$$g_{m1} = 15 \text{ mS} \rightarrow \left(\frac{g_m}{I_D} \right)_1 = 12$$

$$A_v = g_{m1} R_{\text{out}} = 2 \rightarrow R_{\text{out}} = 134 \Omega$$

$$\frac{1}{g_{m2}} = 150 \Omega \rightarrow g_{m2} = 6.7 \text{ mS} \rightarrow \left(\frac{g_m}{I_D} \right)_2 = 5.3$$

$$R_{\text{out}} = \frac{R_{D1} \cdot r_{o1}}{R_{D1} + r_{o1}} = 134 \rightarrow r_{o1} \geq 1257 \Omega \rightarrow \left(\frac{g_m}{g_{ds}} \right)_1 \geq 19$$

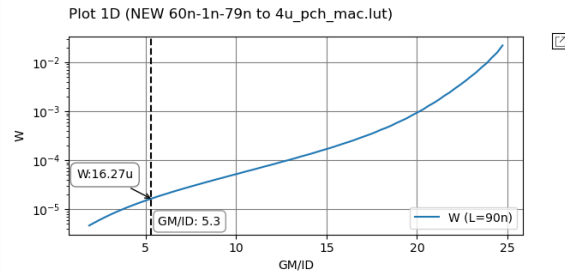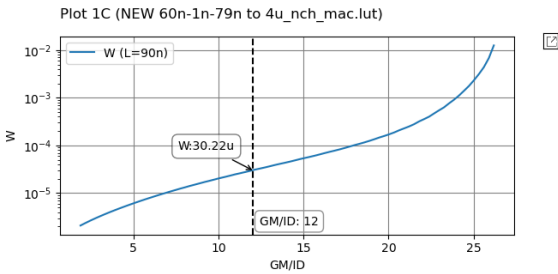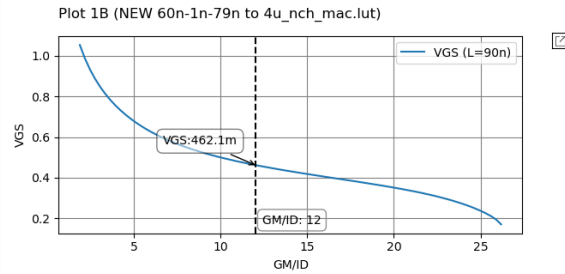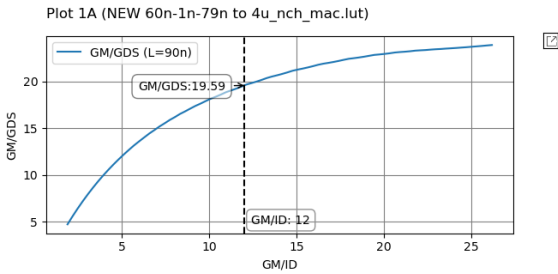
$$\text{Assume } V_{\text{out}} = 600 \text{ mV and } L_1 = L_2$$



$$L = 90 \text{ nm}, V_{GS1} = 462.1 \text{ mV}, W_1 = 30.22 \text{ um}, W_2 = 16.27 \text{ um}$$

Apply Results to Cadence

DC - OP

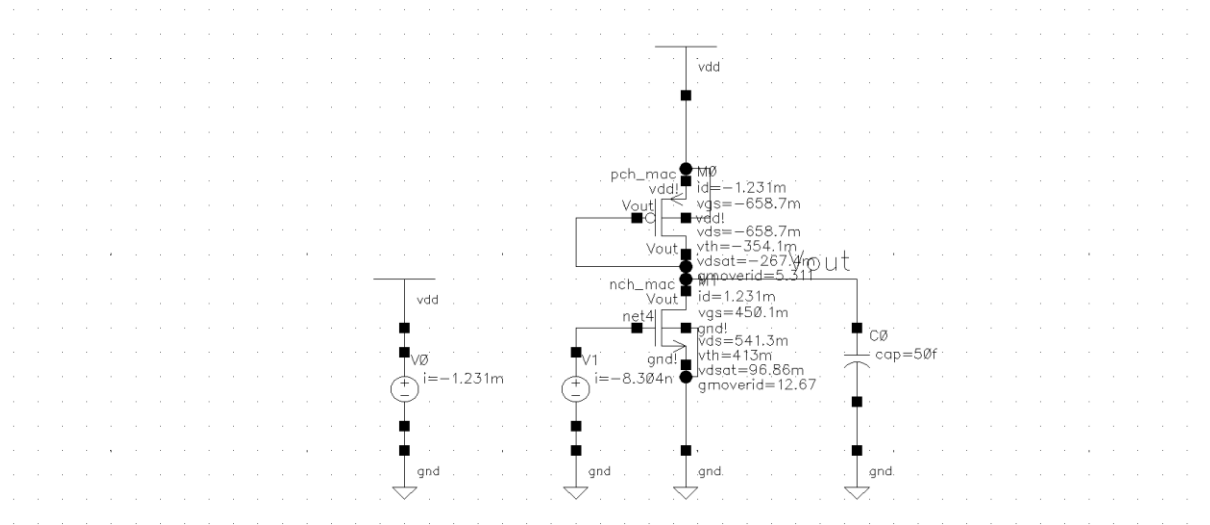

AC Analysis

