

Build a common gate amplifier that meets the following specs

Spec.	
DC Gain	20 dB
BW	≥ 14 MHz
Power Consumption	≤ 70 uW
Cap Load	1 pF

$$P_{\text{cons}} = V_{\text{DD}} I_D \leq 70 \text{ uW} \rightarrow I_D \leq 58 \text{ uA}$$

$$\text{GBW} = \frac{g_m}{2\pi C_{\text{out}}} \geq 10 * 14 \text{ MHz} \rightarrow g_m \geq 880 \text{ uS} \rightarrow g_m = 1.05 \text{ mS} \rightarrow \frac{g_m}{I_D} = 18.1$$

$$A_v = g_m R_{\text{out}} = 10 \rightarrow R_{\text{out}} = 9.6 \text{ k}\Omega \rightarrow R_D = 11.5 \text{ k}\Omega \rightarrow r_o \geq 58.1 \text{ k}\Omega \rightarrow \frac{g_m}{g_{ds}} \geq 61$$


$$V_{\text{out}} = V_{\text{DD}} - I_D * R_D = 1.2 - 58\text{u} * 11.5\text{k} = 0.533 \text{ V}$$

Assume V_{out} divided equally between M1 and M2


$$L_1 = 840 \text{ nm}, V_{\text{GS1}} = 373.8 \text{ mV}, W_1 = 44.71 \text{ um}$$

For the Current source device assume long L and bias it in SI ($gm_{\text{overid}} = 10$) to achieve large output resistance
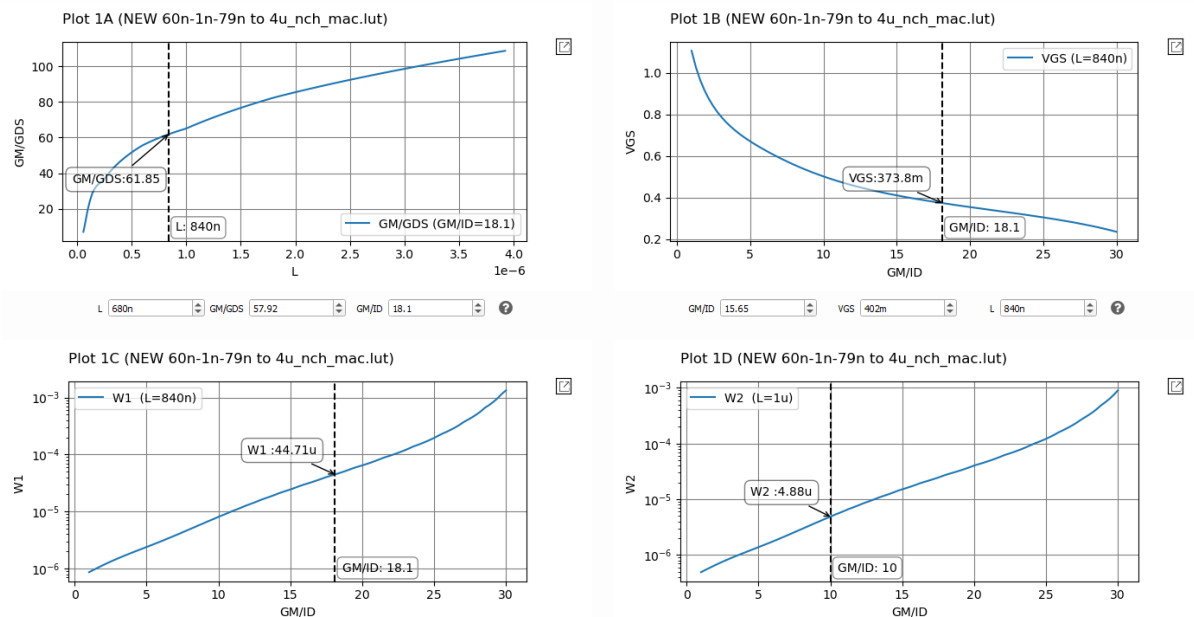
$$L_2 = 1 \text{ um}, W_2 = 4.88 \text{ um}$$



1. DC Operating Points

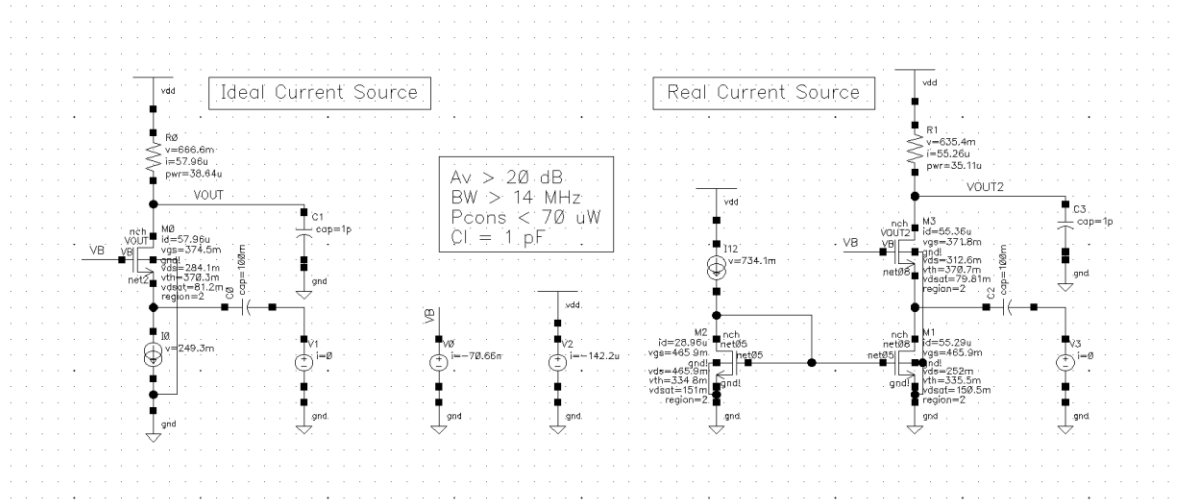

2. AC Analysis

