


General Parameters

A_{ol}	$1e4 = 80 \text{ dB}$
UGF	10 MHz
R_{FB}	9 K Ω (4K, 9K for parametric sweep)
R	1 K Ω
DC input	1 V
ac input	sine wave : 1 V amplitude and 1 KHz frequency
time step	period/50

Deliver 1 : Op-Amp Subcircuit

Op-Amp model has three basic stages

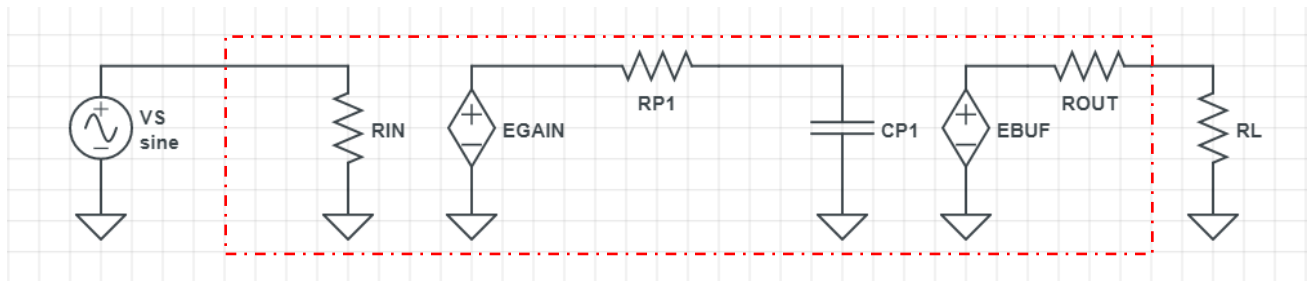1. diff amplifier with high voltage gain - R_{IN} , $EGAIN$
2. A single pole low pass filter - R_{P1} , C_{P1}
3. An output buffer - $EBUF$, R_{OUT}



Hand Analysis :

As A_{ol} is provided by $EGAIN = A_{ol} = 10^4 = 80 \text{ dB}$ and the first pole

Fig1. Op-Amp Sub-Circuit

frequency f_{p1} is given by the relation [1]

$$f_{p1} = \frac{1}{2\pi R_{p1} C_{p1}} = \frac{UGF}{A_{ol}} \quad [1]$$

and with $A_{ol} = 10^4$ and $UGF = 10 \text{ MHz}$ the cut off frequency $f_{p1} = 1 \text{ KHz}$

choose $R_{p1} = 1 \text{ K}\Omega$

$$\therefore C_{p1} = \frac{10^4}{10 * 10^6} * \frac{1}{2\pi * 1K} = 0.15915 \text{ uF}$$

Assume $R_{IN} = 100 \text{ M}\Omega$ and $R_{OUT} = 10 \Omega$ and $R_L = 1 \text{ K}\Omega$

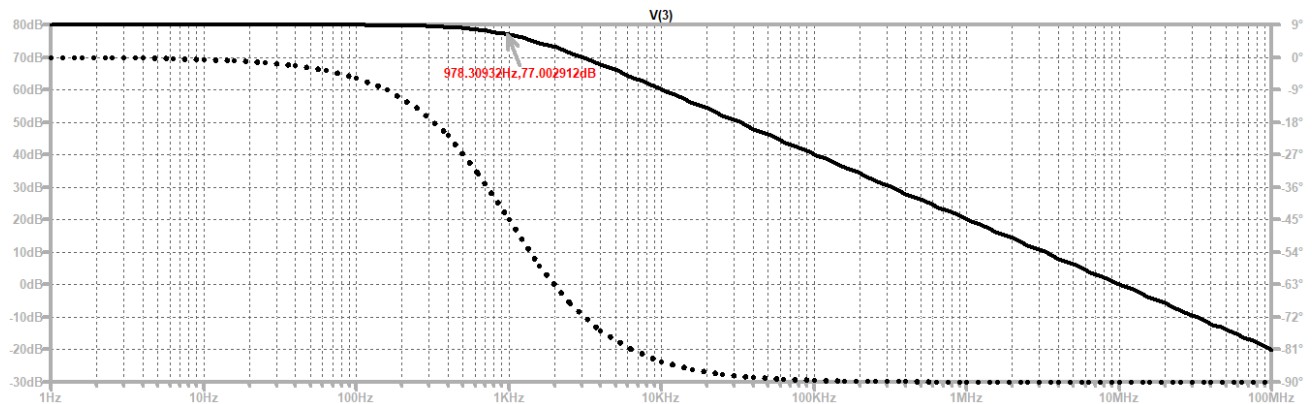


Fig.2. Op-Amp Model AC analysis

Sub-Circuit Netlist

```
SpiceOPAMP.CIR
*
* use ac input sine wave with 1V peak value and f = 1 KHz
VS 1 0 AC 1 SIN(0VOFF 1VPEAK 1KHZ)
* Define the model terminals
XOP 1 0 3 OPAMP
* use 1 Kohm as load resistance
RL 3 0 1k
*
* OPAMP MACRO MODEL, SINGLE-POLE
* connections:      non-inverting input
*                   |      inverting input
*                   |      |      output
*                   |      |      |
.SUBCKT OPAMP      1      2      6
* INPUT IMPEDANCE
RIN 1 2 100MEG
* DC GAIN=10K AND UNITY GAIN=10MHZ
* UNITY GAIN = DCGAIN X POLE1
EGAIN 3 0 1 2 10K
* assume Rpl = 1K
RP1 3 4 1K
* POLE1 = 1/(2*pi*RP1*CP1)
CP1 4 0 0.15915UF
* OUTPUT BUFFER AND RESISTANCE
EBUFFER 5 0 4 0 1
ROUT 5 6 10
.ENDS
*
* ANALYSIS
.AC DEC 5 1 100MEG

.END
```