

You are required to design a single ended amplifier (choose the common source with resistive load amplifier) to achieve the following specs

Spec.	
DC Gain	6 dB
BW	$\geq 10 \text{ GHz}$
Power Consumption	$\leq 1.2 \text{ mW}$
Cap Load	50 fF

1. Design

$$P_{\text{cons}} = V_{DD} I_D \leq 1.2 \text{ mW} \rightarrow I_D \leq 1 \text{ mA}$$

$$GBW = \frac{g_m}{2\pi C_{\text{out}}} \geq 2 * 10 \text{ GHz} \rightarrow g_m \geq 6.3 \text{ mS}$$

$$\text{let } g_m = 9 \text{ mS} \rightarrow \frac{g_m}{I_D} = 9$$


$$A_v = g_m R_{\text{out}} = 2 \rightarrow R_{\text{out}} = 225 \Omega$$

$$R_D = 270 \Omega \rightarrow R_{\text{out}} = \frac{R_D \cdot r_o}{R_D + r_o} = 225 \rightarrow r_o \geq 1350 \Omega \rightarrow \frac{g_m}{g_{ds}} \geq 12.15$$

$$V_{DS} = V_{\text{out}} = V_{DD} - I_D \cdot R_D = 1.2 - 1\text{m} \cdot 270 = 930 \text{ mV}$$


$$V_{SB} = 0$$

From g_m/I_D Charts

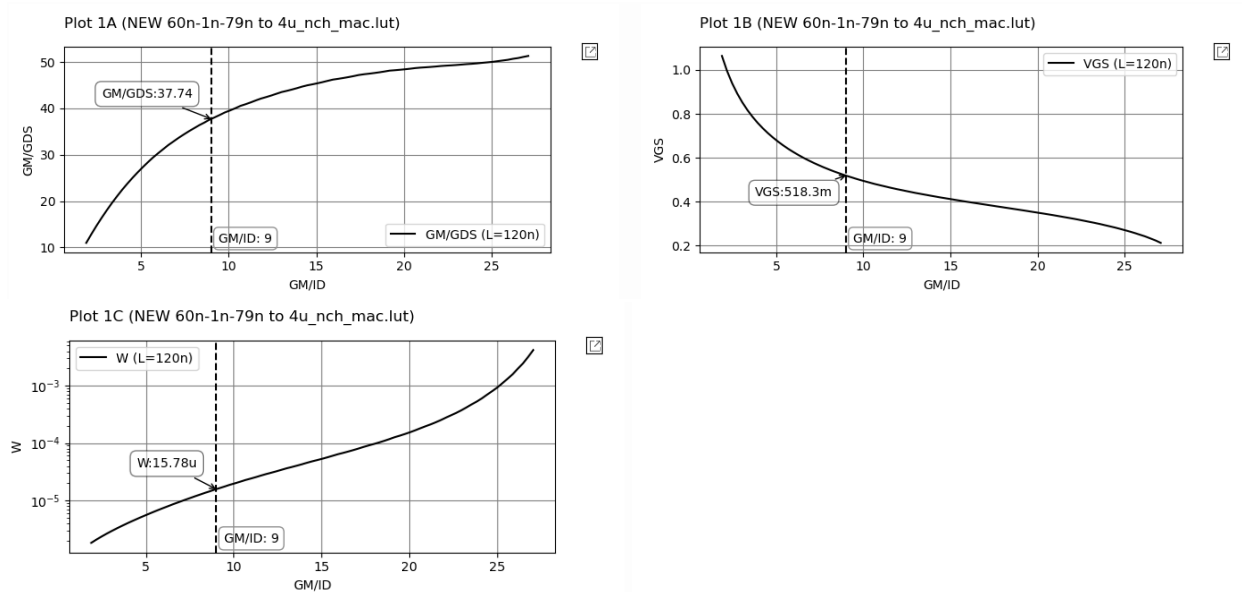

2. Simulations

- DC OP

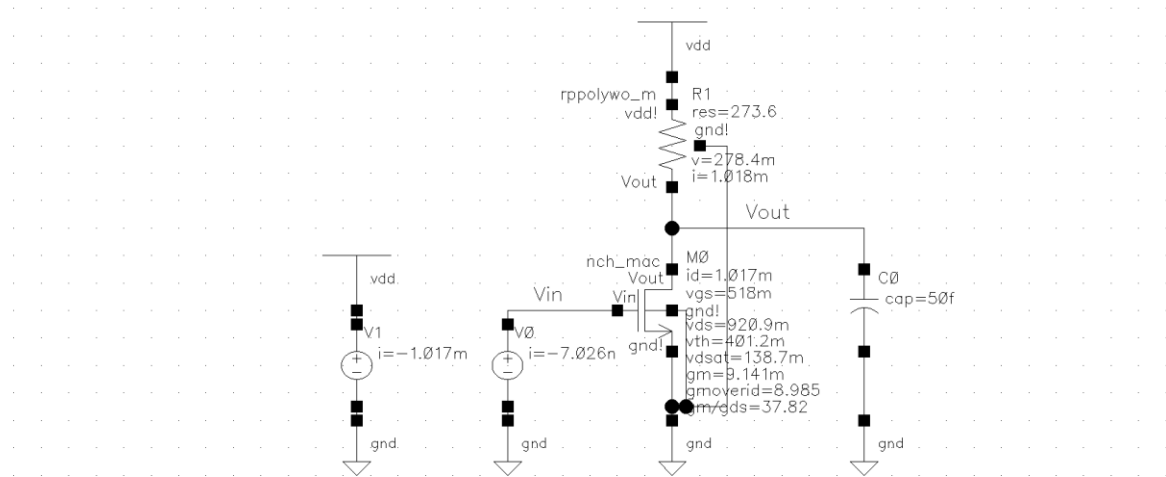

- AC Analysis

