

Design a single ended amplifier (choose common source with resistive load) to achieve the following specs

Spec.	
DC Gain	20 dB
BW	$\geq 1 \text{ GHz}$
Power Consumption	$\leq 0.5 \text{ mW}$
Cap Load	50 fF

1. Design (Using gmoverid charts)

$$P_{\text{cons}} = V_{DD} I_D \leq 0.5 \text{ mW} \rightarrow I_D \leq 400 \mu\text{A}$$




$$GBW = \frac{g_m}{2\pi C_{\text{out}}} \geq 10 * 1 \text{ GHz} \rightarrow g_m \geq 3.14 \text{ mS}$$

$$\text{Assume } V_{\text{out}} = 0.6 \rightarrow \text{maximum output swing} \rightarrow R_D = \frac{1.2 - 0.6}{400 \mu} = 1500 \Omega$$

$$\text{Assume } R_{\text{out}} = 1200 \Omega \rightarrow R_{\text{out}} = \frac{R_D \cdot r_o}{R_D + r_o} = 1200 \rightarrow r_o \geq 6000 \Omega$$


$$A_v = g_m R_{\text{out}} = 10 \rightarrow g_m = 8.33 \text{ mS} \rightarrow \frac{g_m}{I_D} = 20.83$$

$$\frac{g_m}{g_{ds}} \geq 50$$

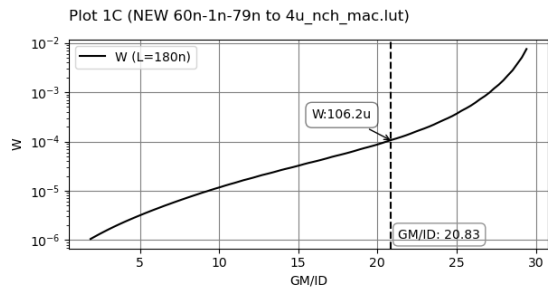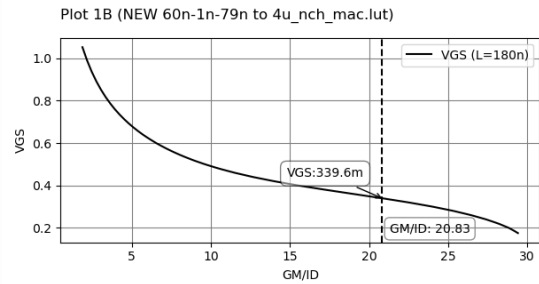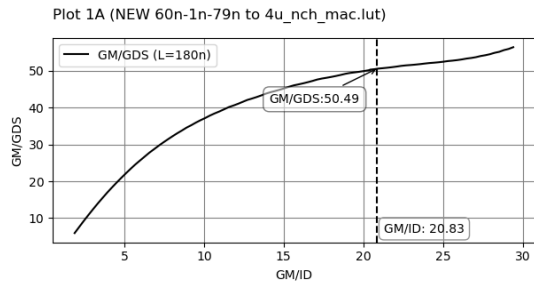

2. Simulations

- DC OP

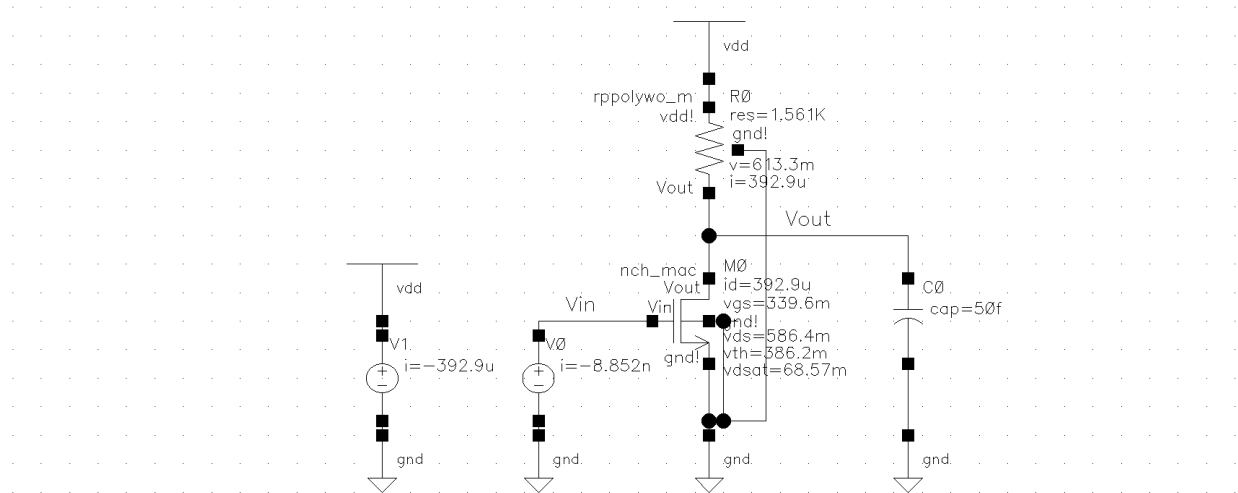

- AC Analysis

AC Analysis 'ac': freq = (1 Hz -> 100 GHz)

1

