

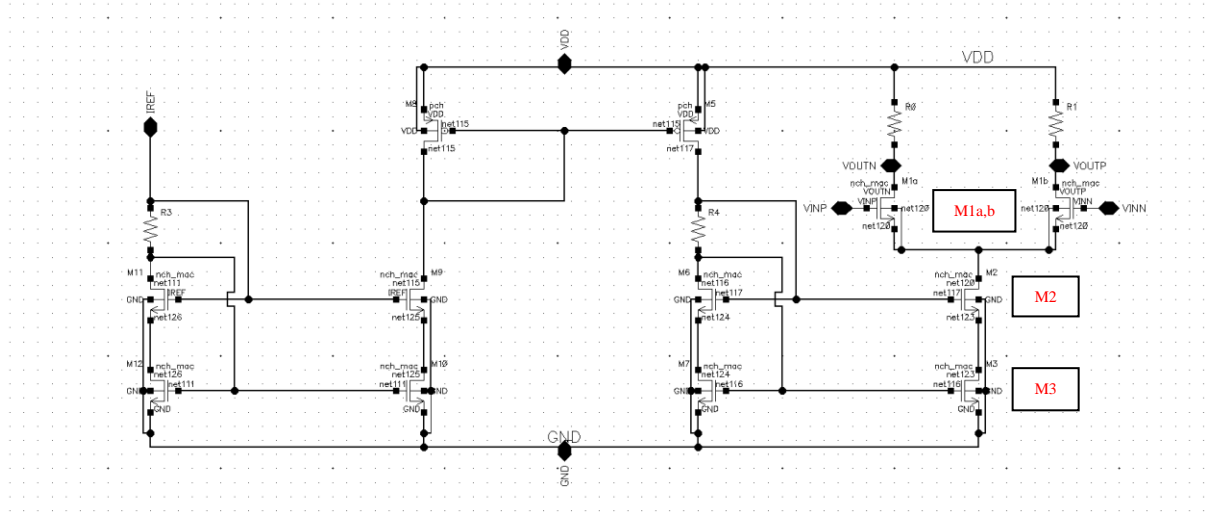
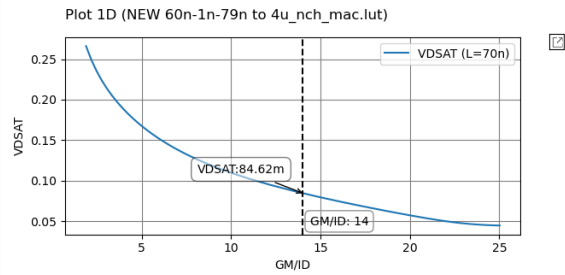
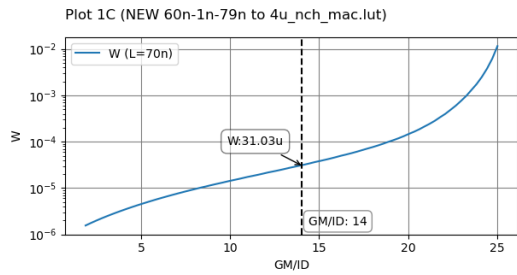


Use gm/ID methodology to design a diff input diff output operational transconductance amplifier (OTA) that achieves the following specs.

Spec.			
DC Gain	0 dB	Linear Range	300 mVpp
BW	≥ 15 GHz	CMRR	≥ 40 dB
Power Consumption	≤ 2.5 mW	Cap Load	100 fF
Reference Current	10 μ A		

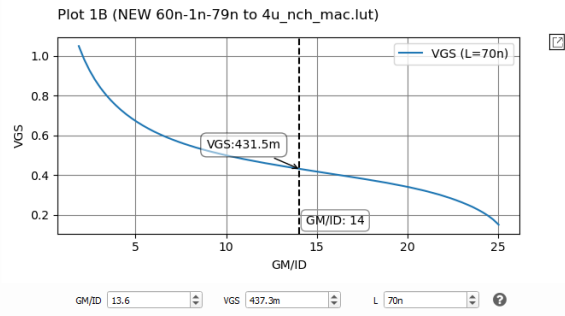

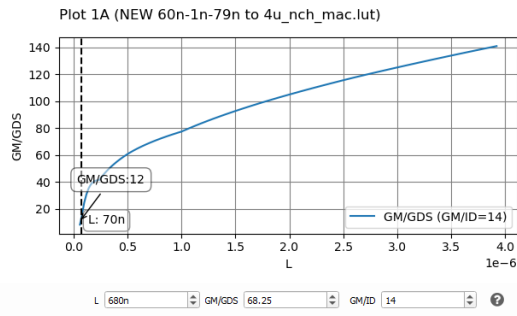

Designing the Current Mirror circuit

$$I_{SS \max} = 2 \text{ mA} = a1 * a2 * I_{REF} \rightarrow a1 * a2 = 200 \rightarrow \text{Choose } a1 = 20 \text{ and } a2 = 10$$

$$CMRR = 2g_m * R_{SS} = 100 \rightarrow R_{SS} \geq 4.4 \text{ k}\Omega \rightarrow R_{SS} = 4.5 \text{ k}\Omega$$





$$\text{use } L_{CM} = 3 * L_{\min} = 180 \text{ nm} \rightarrow \text{reduce } \frac{1}{f} \text{ noise and bias it in SI: } \left(\frac{g_m}{I_D} \right)_3 = 10$$

$$W_3 = 64.84 \text{ um}, r_{o3} = 901.3 \text{ }\Omega, V_{GS3} = 493.2 \text{ mV}$$

$$(g_m \cdot r_o)_2 = 5 \rightarrow L_2 = 60 \text{ nm}$$


$$\text{Assume } V_{GS2} = V_{GS3} = 493.2 \text{ mV} \rightarrow W_2 = 36.86 \text{ um}$$
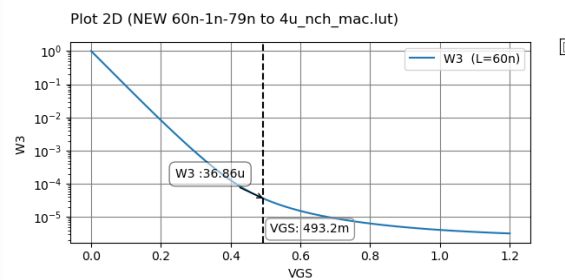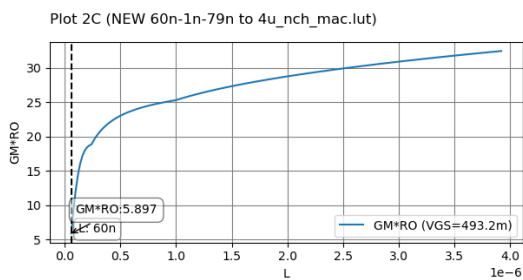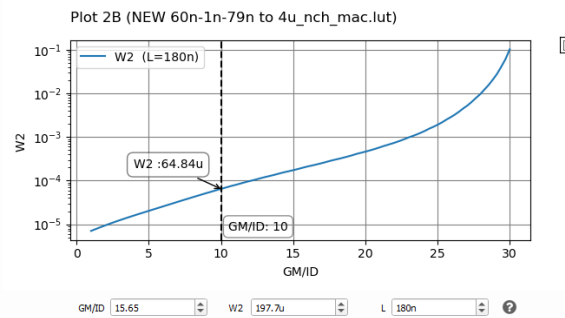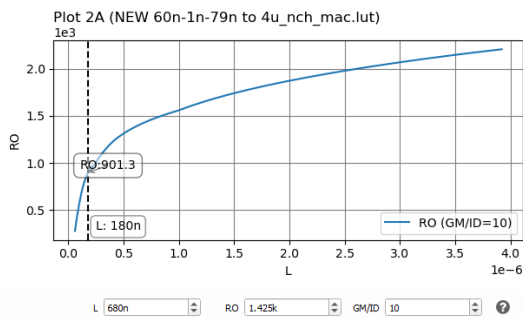
$$\text{For } R_{CM} = \frac{V_{DS3}}{I_{ref}} = 25000$$




Simulations


DC OP

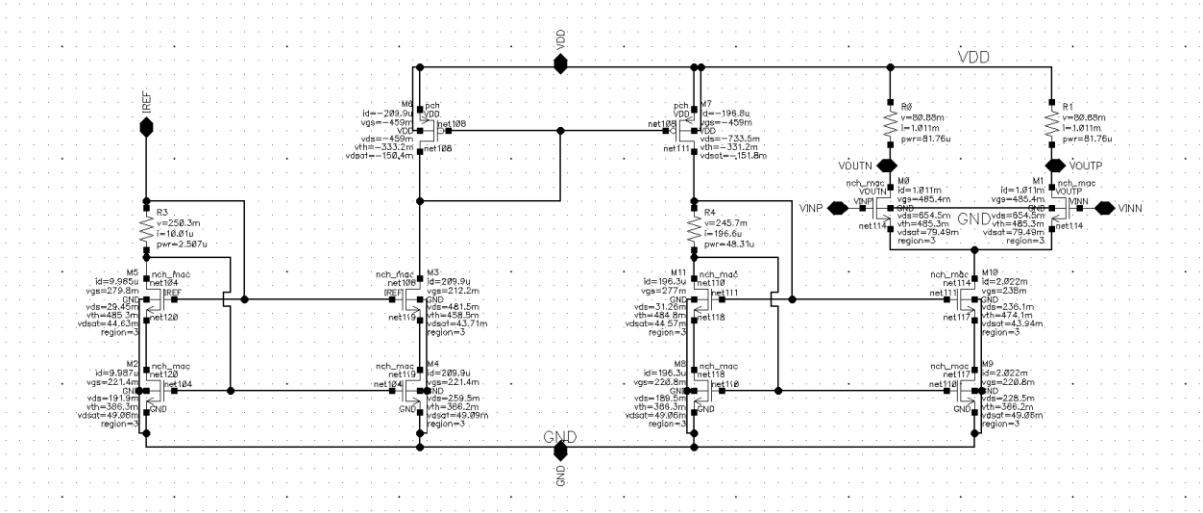

Av Differential

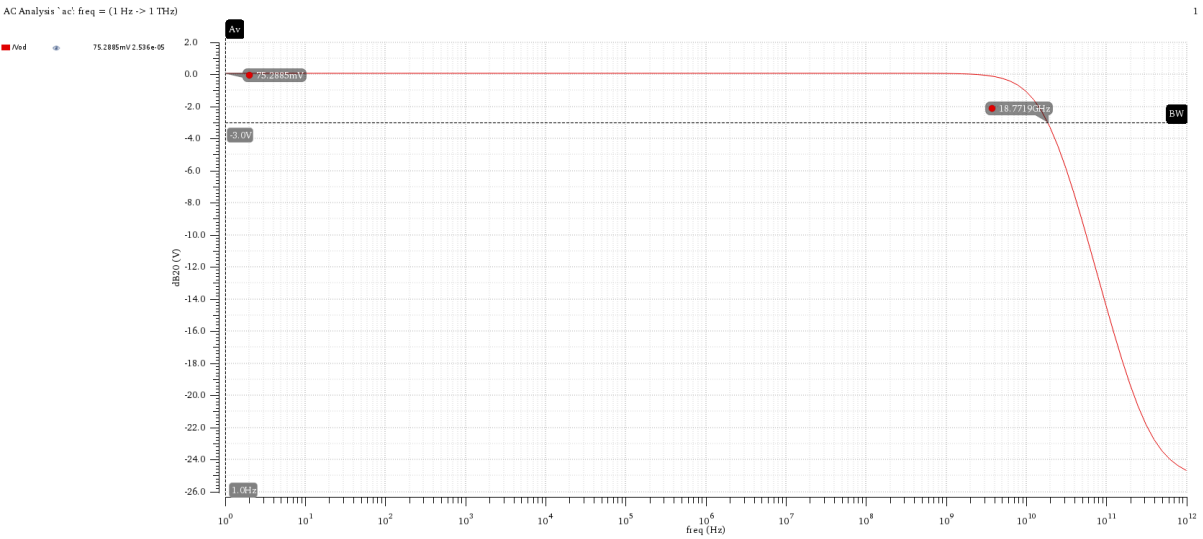

CMRR

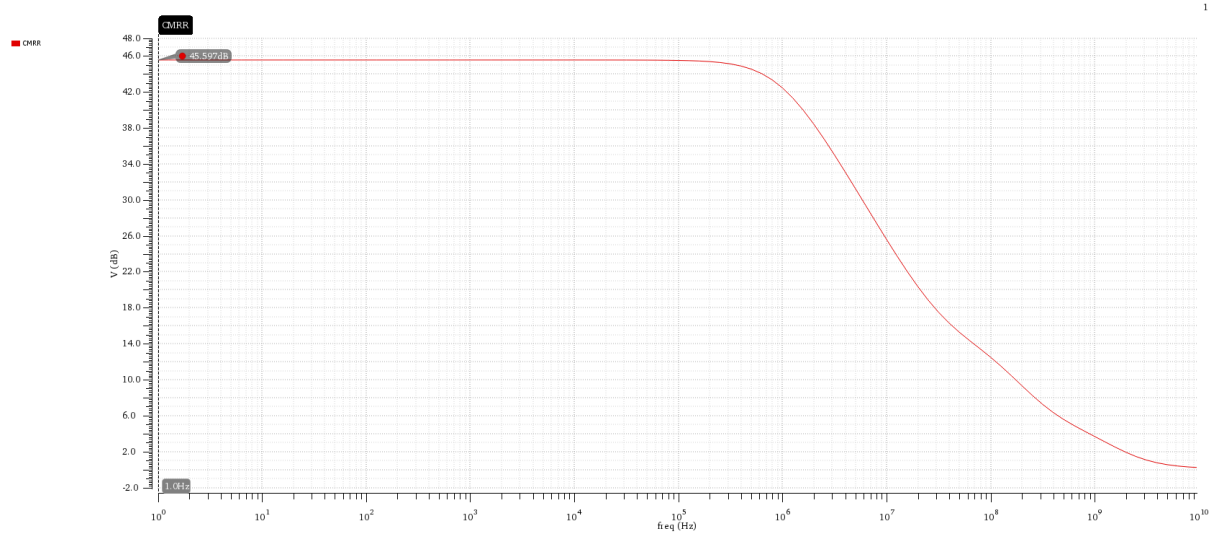

CMIR

