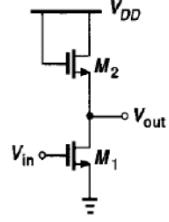


Design a single ended amplifier shown in the fig to achieve the following specs

Spec.		
DC Gain	6 dB	
BW	≥ 10 GHz	
Power Consumption	≤ 1.5 mW	
Cap Load	50 fF	

$$P_{\text{cons}} = V_{DD} I_D \leq 1.5 \text{ mW} \rightarrow I_D \leq 1.25 \text{ mA}$$

$$GBW = \frac{g_{m1}}{2\pi C_{\text{out}}} \geq 2 * 10 \text{ GHz} \rightarrow g_{m1} \geq 6.28 \text{ mS}$$





$$g_{m1} = 18 \text{ mS} \rightarrow \left(\frac{g_m}{I_D}\right)_1 = 14.4$$

$$A_v = g_{m1} R_{\text{out}} = 2 \rightarrow R_{\text{out}} = 115 \Omega$$

$$R_{D1} = \frac{1}{g_{m2}} = 127 \Omega$$

$$R_{\text{out}} = \frac{R_{D1} \cdot r_{o1}}{R_{D1} + r_{o1}} = 115 \rightarrow r_{o1} \geq 1220 \Omega \rightarrow \frac{g_m}{g_{ds}} \geq 22$$

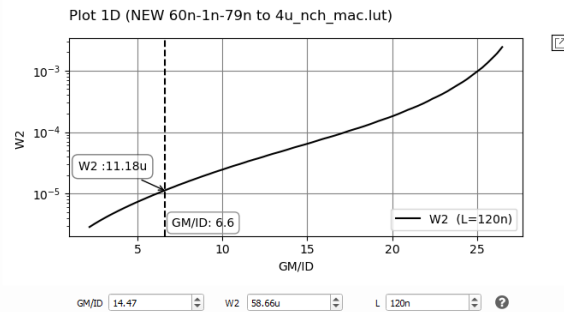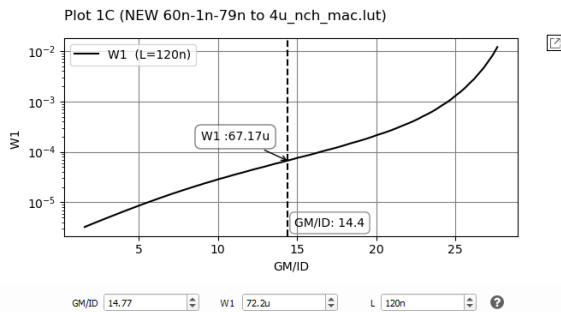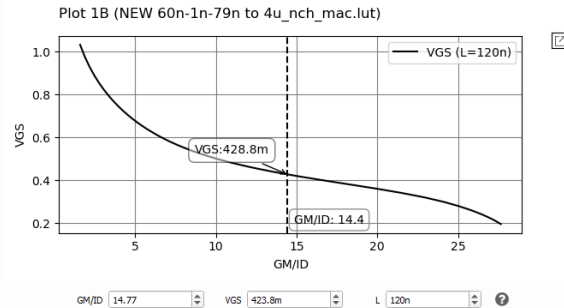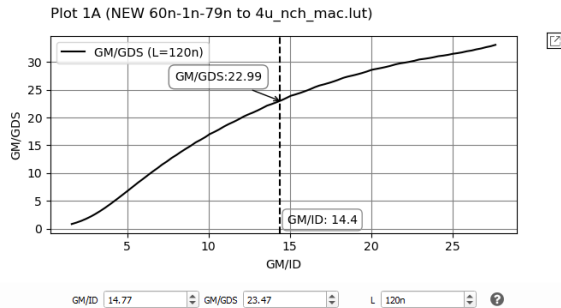
$$\text{Assume } V_{\text{out}} = 300 \text{ mV and } L_1 = L_2$$



With some fine tuning W2 reduced to 9.67 um, and VGS to 421.5 mV

Apply to Cadence

1. DC OP

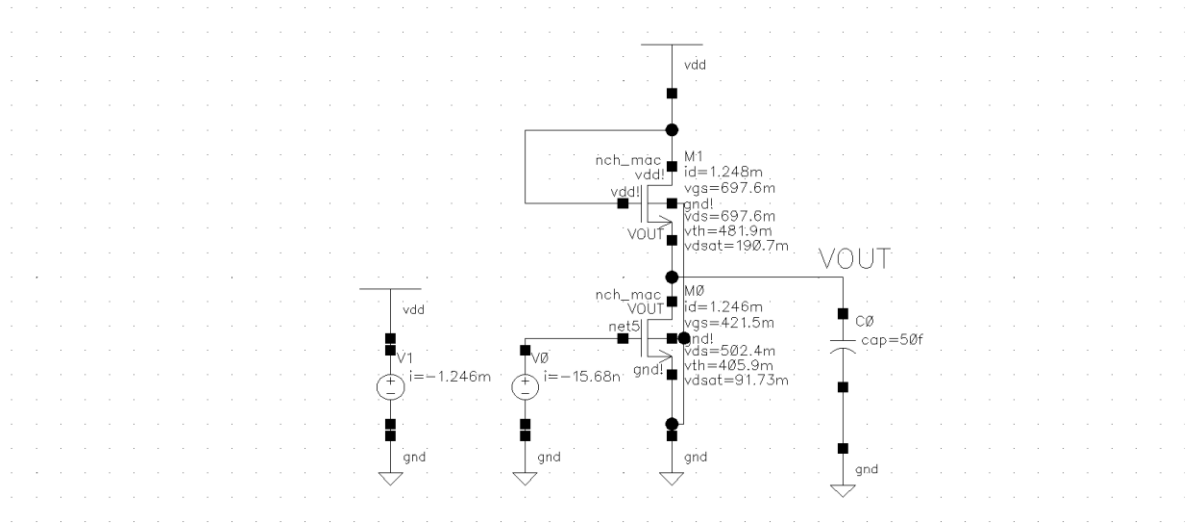

2. AC Analysis

