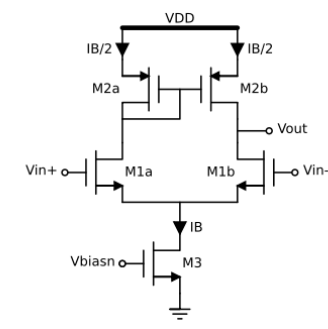


Use gm/ID methodology to design a diff input SE output operational transconductance amplifier (OTA) that achieves the following specs.

Spec.			
Supply Voltage	1.2 V		
Open loop DC voltage gain	≥ 32 dB		
CMRR @ DC	≥ 70 dB		
BW	≥ 200 kHz		
Phase Margin	$\geq 70^\circ$		
Power Consumption	≤ 30 uW		
Reference current	10 uA		
CM input range low	≤ 0.6 V		
CM input range high	≥ 1 V		
Load	2 pF		





1. As CMIR : 0.6 to 1v is closer to VDD, I used a NMOS input transistors
2. Design of input transistors

$$P_{\text{cons}} = V_{\text{DD}} I_{\text{SS}} \leq 30 \text{ uW} \rightarrow I_{\text{SS}} \leq 20 \text{ uA}$$

$$\text{GBW} = \frac{g_{m1}}{2\pi C_L} \geq 8 \text{ MHz} \rightarrow g_{m1} \geq 100.5 \text{ uS} \rightarrow g_m = 120 \text{ uS} \rightarrow \frac{g_m}{I_D} = 12$$

$$A_v = g_m R_{\text{out}} = 40 \rightarrow R_{\text{out}} = 335 \text{ k}\Omega \rightarrow R_{\text{out}} = r_{o1} || r_{o2} = \frac{r_o}{2} \rightarrow r_o = 670 \text{ k}\Omega$$

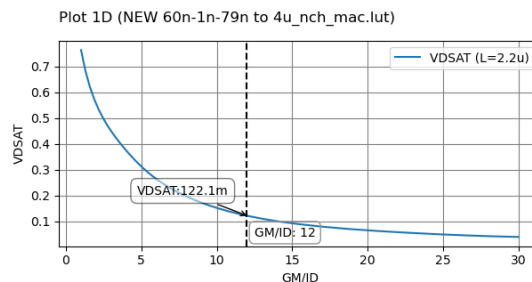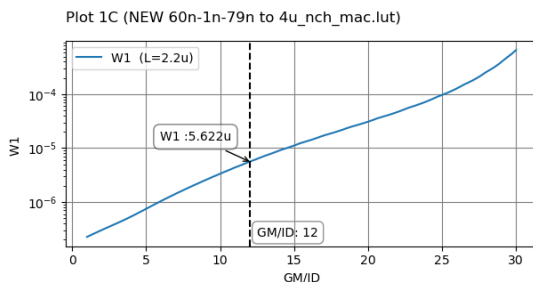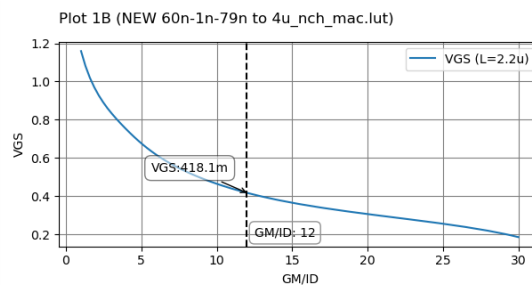
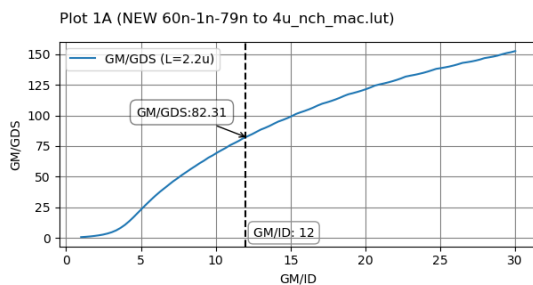
$$L_1 = 2.2 \text{ um}, V_{\text{GS1}} = 418.1 \text{ mV}, W_1 = 5.63 \text{ um}$$



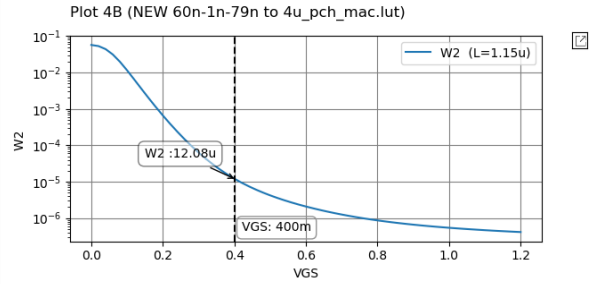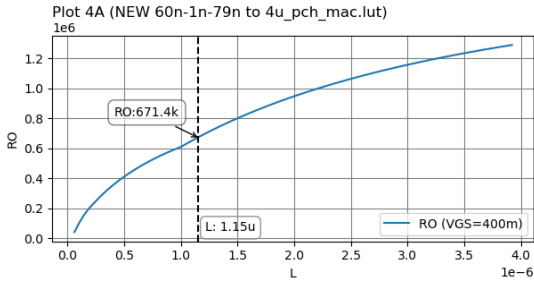3. Diode connected load

$$\text{CMIR}_H \geq 1 \rightarrow V_{GS1} - V_1^* - V_{SG2} + V_{DD} \geq 1 \rightarrow V_{SG2} \leq 452\text{m}$$

$$V_{SG2} = 400\text{m and } r_{o2} = 670\text{ k}\Omega \rightarrow L_2 = 1.15\text{ }\mu\text{m}, W_2 = 12.08\text{ }\mu\text{m}$$





4. Current mirror


$$A_{\text{VCM}} = \frac{1}{2g_m R_{ss}} = (70 - 32)\text{ dB} = 0.01259 \rightarrow R_{ss} = 331\text{ k}\Omega$$

$$\text{CMIR}_L < 0.6 \rightarrow V_{GS1} + V_3^* \leq 0.6 \rightarrow V_3^* \leq 0.189 \rightarrow V_3^* = 0.17 \rightarrow \left(\frac{g_m}{I_D}\right)_3 = 11.76$$

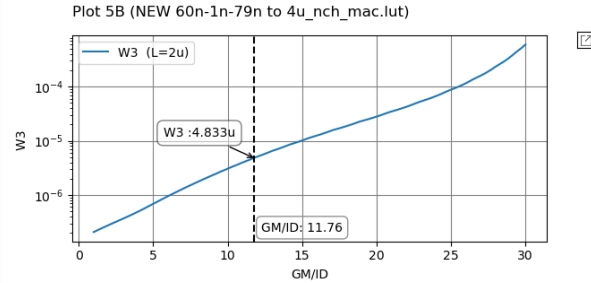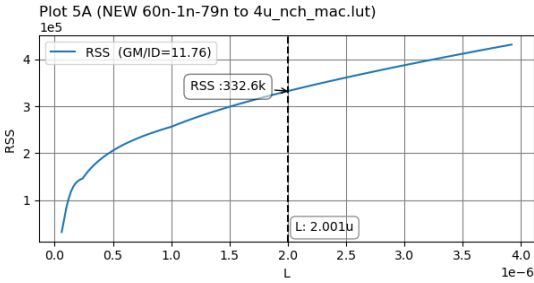
$$L_3 = 2\text{ }\mu\text{m}, W_3 = 4.833\text{ }\mu\text{m}$$




1. Circuit Test Bench

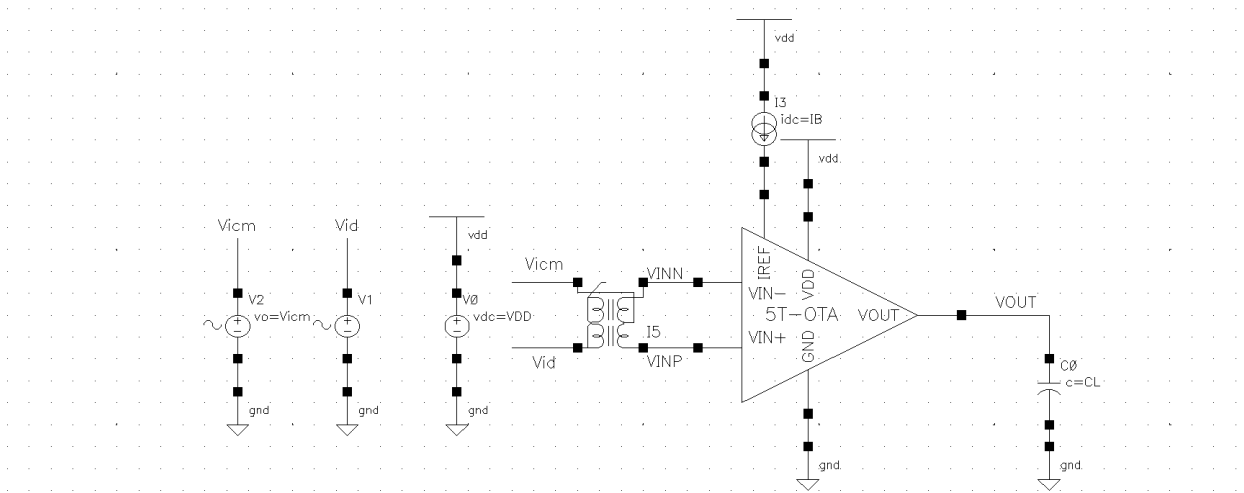


2. DC OP

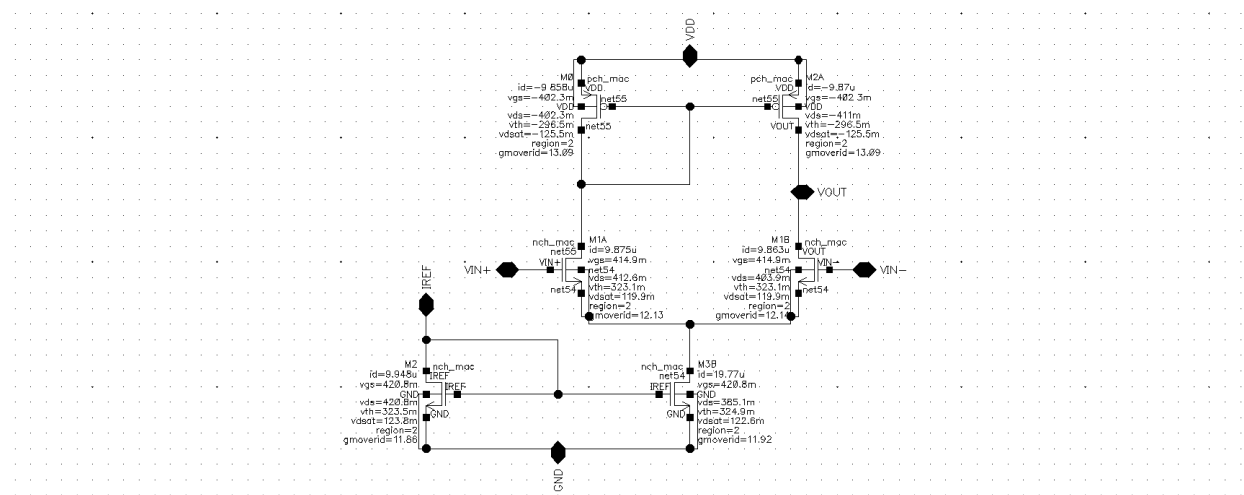


3. Diff Small Signal Analysis

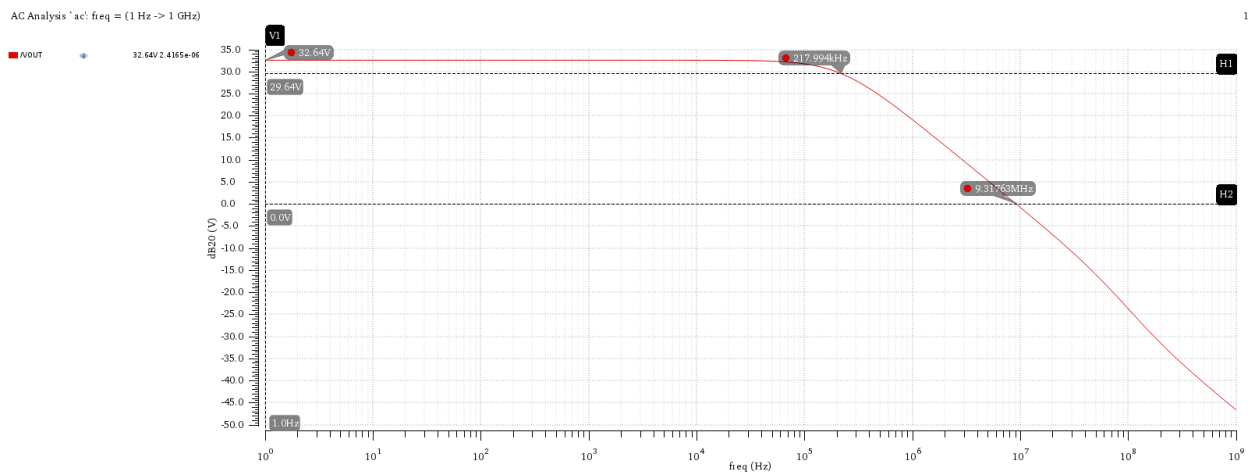

4. CM Small Signal Analysis

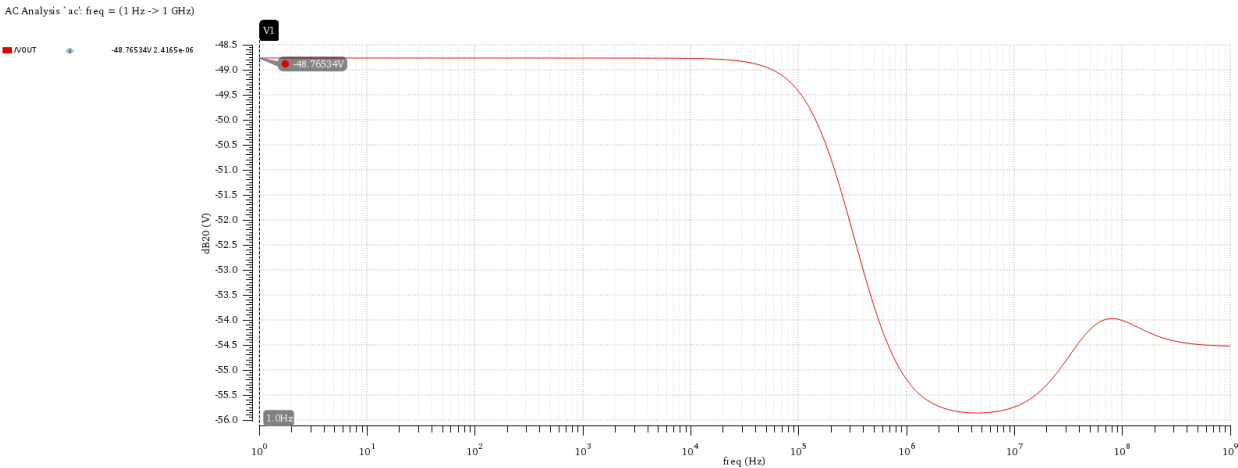

5. Diff Large Signal

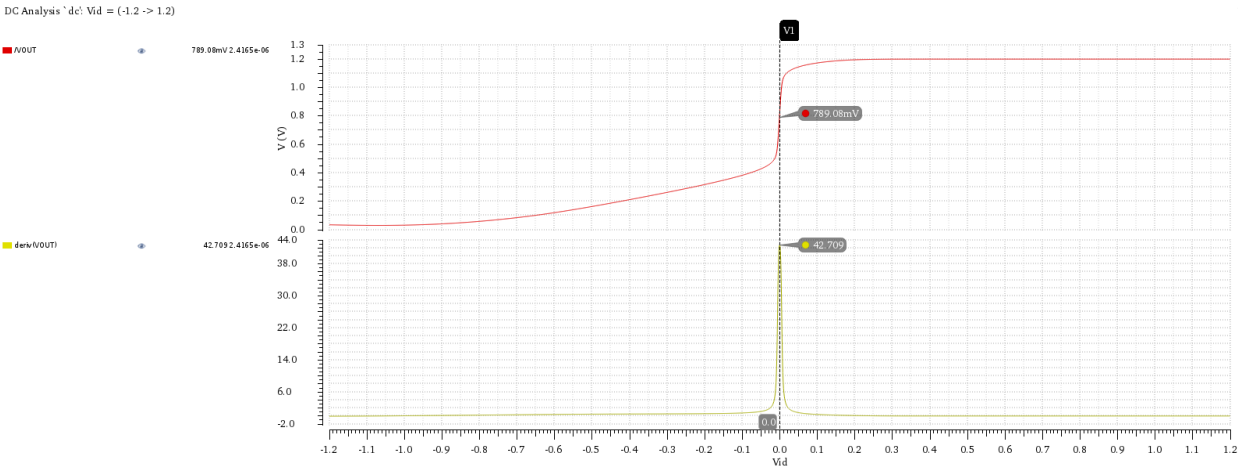

6. CM Large Signal

