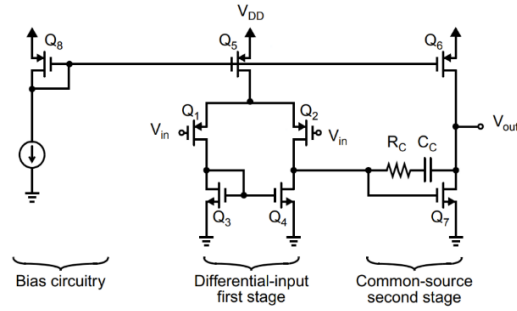


Design a Single Ended Two Stage Miller Compensated OTA meets the Specs (Use IREF = 10u)

Spec.	
DC Gain	≥ 60 dB
Unity Gain Frequency	≥ 50 MHz
Power Consumption	≤ 1 mW
Cap Load	1 pF

- Assume $C_C = 0.5 C_L = 0.5$ pF
- Assume CMIR from 0.2 \rightarrow 0.6 V \rightarrow use PMOS input transistors
- Assign higher gain for the first stage $A_V = A_{V1} \cdot A_{V2} = 40 * 25$







$$I_{Dmax} = \frac{P_{cons}}{V_{DD}} \rightarrow I_{Dmax} \leq 830 \text{ uA}$$

$$UGF = \frac{g_{m1,2}}{2\pi C_C} \geq 50 \text{ MHz} \rightarrow g_{m1,2} \geq 157 \text{ uS} \rightarrow g_{m1,2} = 200 \text{ uS}$$

$$\text{Assume } M_{1,2} \text{ in MI } \left(\frac{g_{m1,2}}{I_D} = 12 \right) \rightarrow I_{D1,2} = 16.7 \text{ uA} \rightarrow I_{B1} = 33.4 \text{ uA}$$

$$A_{V1} = \frac{g_{m1,2} r_{o2,4}}{2} (\text{Assume } r_{o2} = r_{o4}) \geq 40 \rightarrow r_{o2,4} = 400 \text{ k}\Omega \rightarrow (g_m r_o)_{1,2} = 80$$
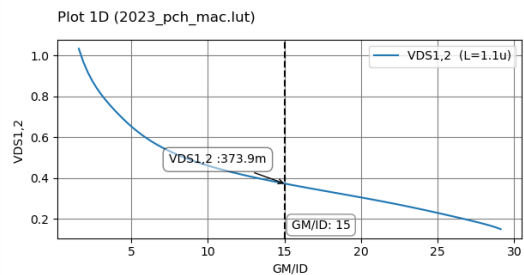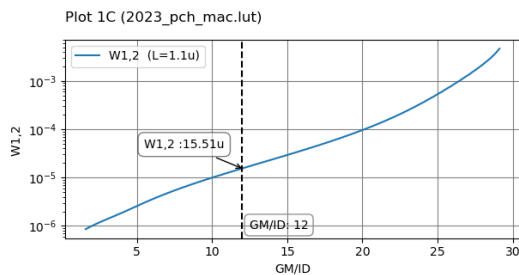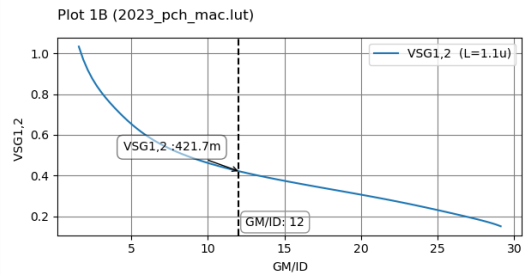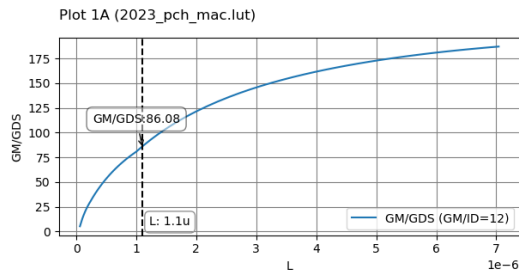
$$L_{1,2} = 1.1 \text{ um}, V_{GS1,2} = 421.7 \text{ mV}, W_{1,2} = 15.51 \text{ um}$$







$$CMIR_L = -V_{SG1,2} + V_{1,2}^* + V_{GS3,4} \leq 0.2 \rightarrow V_{GS3,4} \leq 0.455 \text{ V}$$

$$\text{set } V_{ICM} = \frac{CMIR}{2} = 400 \text{ mV} \rightarrow V_{GS3,4} = 400 \text{ m} + 419.8 \text{ m} - 373.9 \text{ m} = 445.9 \text{ mV} = V_{GS7}$$

$$\text{Choose } \omega_{p2} = 4\omega_u \rightarrow PM > 70^\circ \rightarrow g_{m7} = 8 g_{m1,2} = 1.6 \text{ mS} \rightarrow I_{B2} = 4I_{B1} = 133.6 \text{ uA}$$

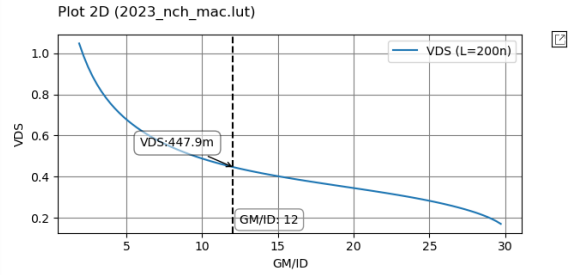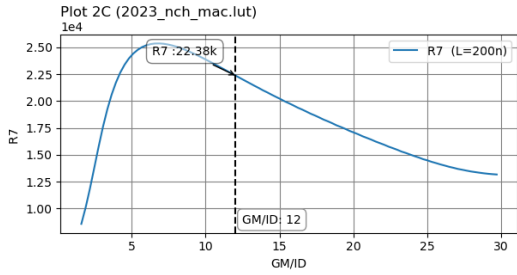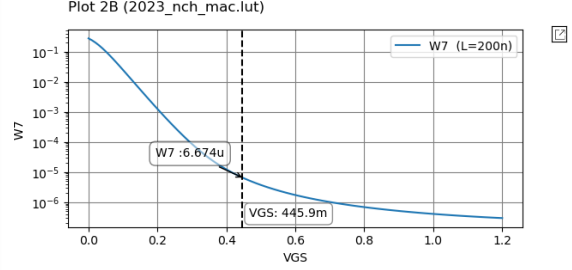
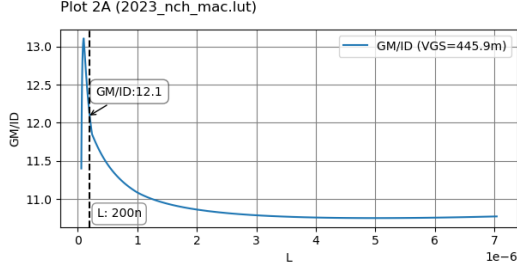
$$L_7 = 200 \text{ nm}, V_{DS7} = 447.7 \text{ mV}, W_7 = 6.674 \text{ um}$$



$$A_{V2} = g_{m7} \left(\frac{r_{o7} * r_{o6}}{r_{o7} + r_{o6}} \right) = 25 \rightarrow r_{o6} = 51.768 \text{ k}\Omega$$



$$CMIR_H = -V_{SG1,2} - V_5^* + V_{DD} \leq 0.6 \rightarrow V_5^* \leq 0.1783 \text{ V} \rightarrow V_5^* = 0.16 \text{ V} \rightarrow \left(\frac{g_{m5,6}}{I_D} \right) = 12.5 \rightarrow g_{m5} = 117.5 \text{ uS}$$
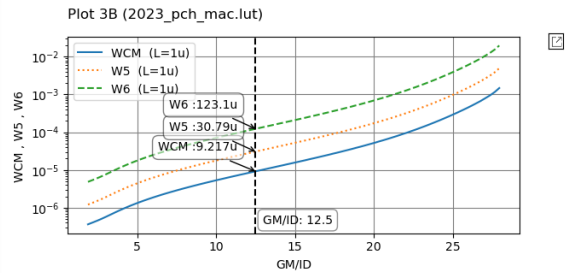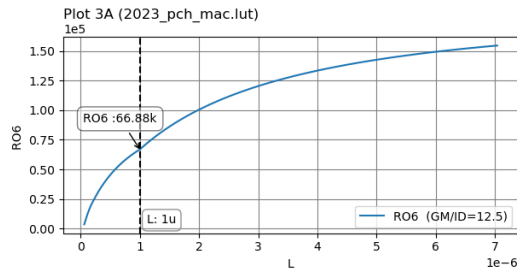
$$L_{CM} = L_5 = L_6 = 1 \text{ um}, W_{CM} = 9.217 \text{ um}, W_5 = 30.79 \text{ um}, W_6 = 123.1 \text{ um}$$



$$r_{o3,4} = r_{o1,2} = 400 \text{ k}\Omega \rightarrow I_{D3,4} = 16.7 \text{ uA} @ V_{GS3,4} = 445.9 \text{ mV}$$
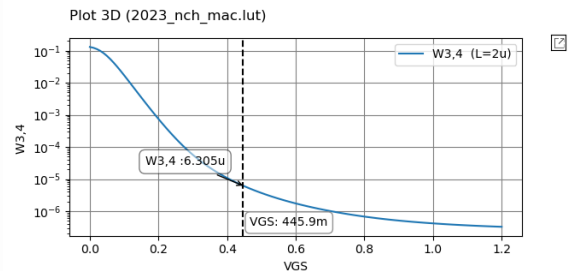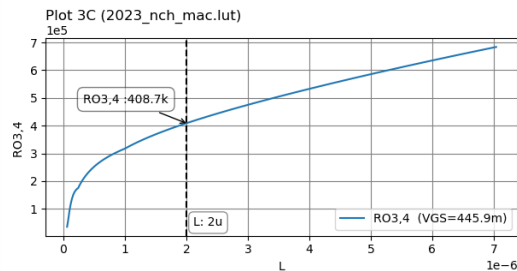
$$L_{3,4} = 2 \text{ um}, W_{3,4} = 6.305 \text{ um}$$



Sizing Summary

	M1	M2	M3	M4	M5	M6	M7	MCM
W	15.51u	15.51u	6.305u	6.305u	30.79u	123.1u	6.674u	9.217u
L	1.1u	1.1u	2u	2u	1u	1u	200n	1u

Simulations Results

